

# Lab 8

## ECE 3300 LAB

### SECTION 02

Instructor: Mohamed Aly

November 22, 2021


### Group I

Name	Bronco ID	Email
Jose Soto-Covarrubias	013778700	jls1@cpp.edu
Shreyas Surana	013790140	ssurana@cpp.edu

## Abstract


Purpose of the experiment was to create a system using up/down counter and barrel shifter. A barrel shifter was used to shift a data by a specified number of bits in one clock cycle in a left rotation or right rotation. In this experiment the number of bits that was used were 32 since 8 displays were used. To create 4-bit barrel shifter, 2 multiplexors were used. The total number of multiplexors used was 8 multiplexors. Similar to lab 5, a button was used as the up/down counter instead of using a switch.


## Theory: Sketch of Design

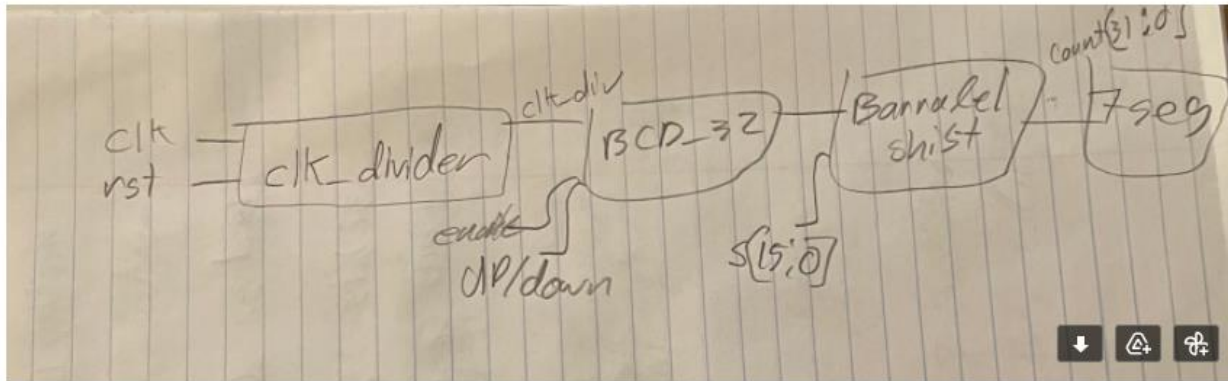


## Area/Resources Information


### Elaborated Design

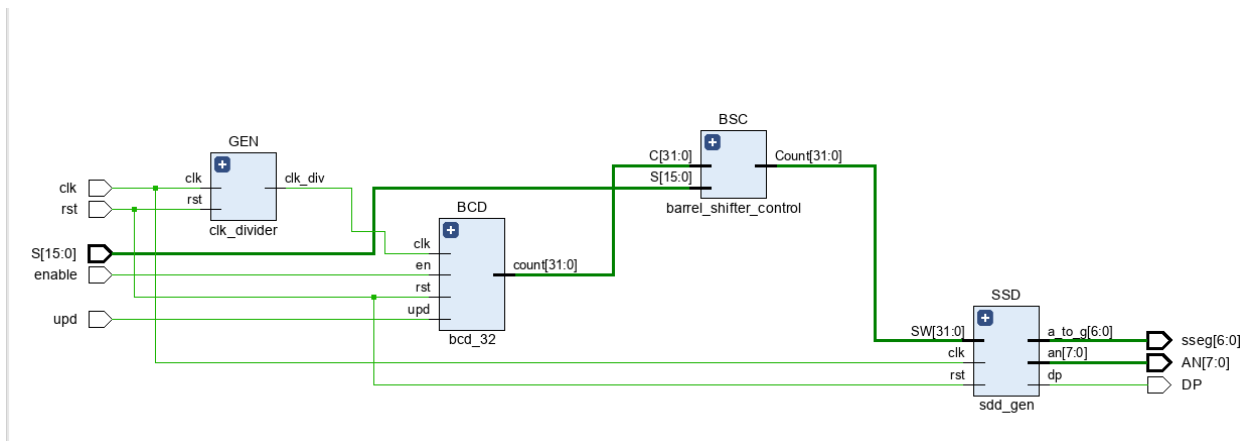


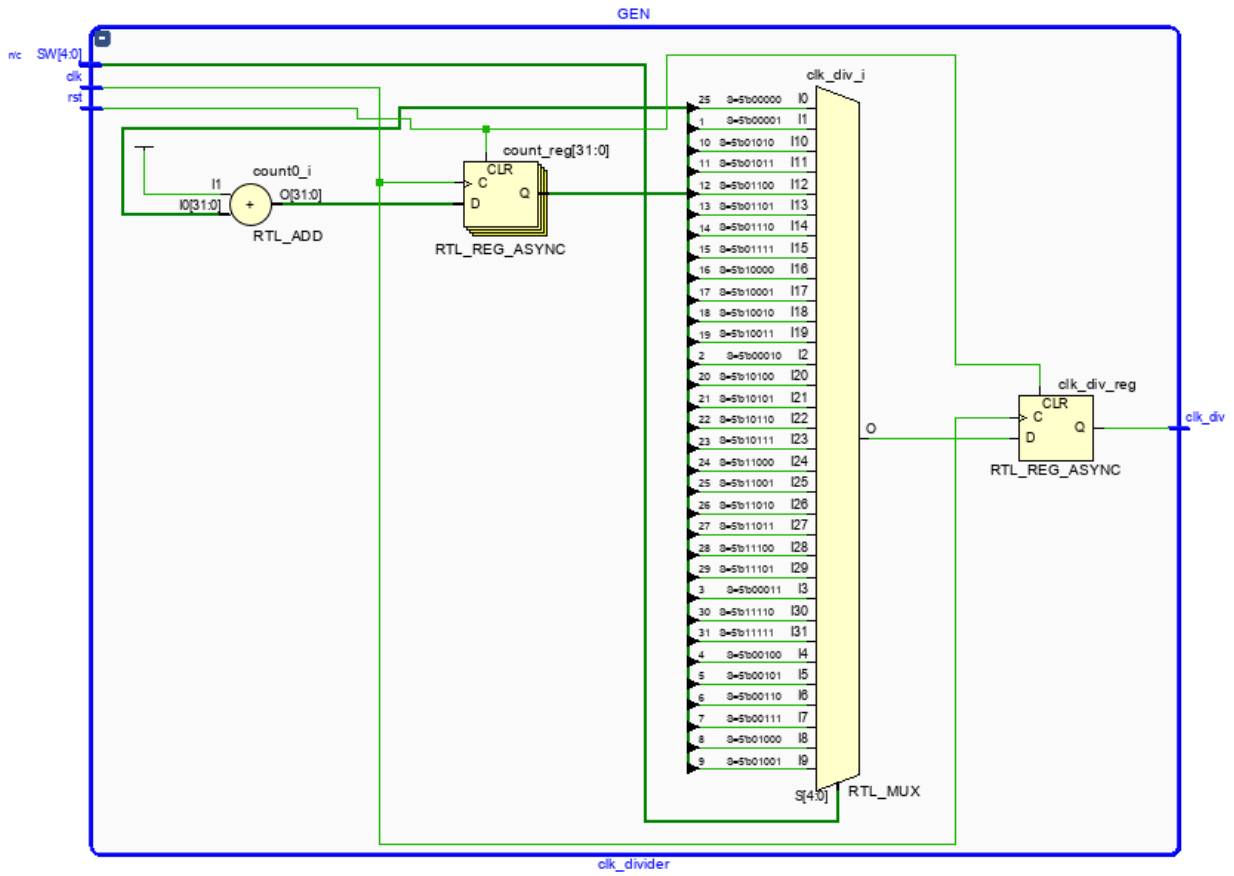

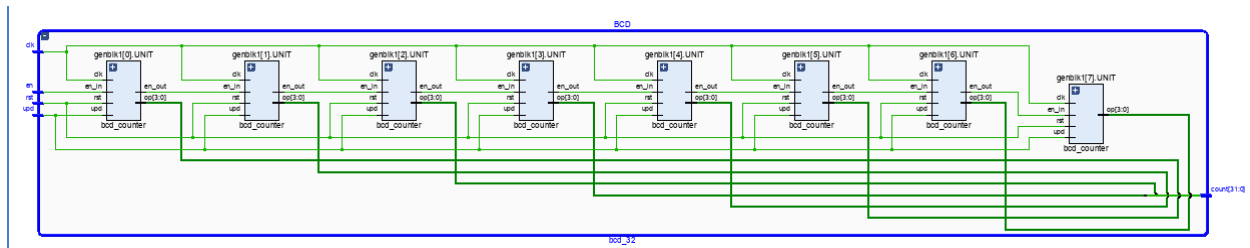



BSC

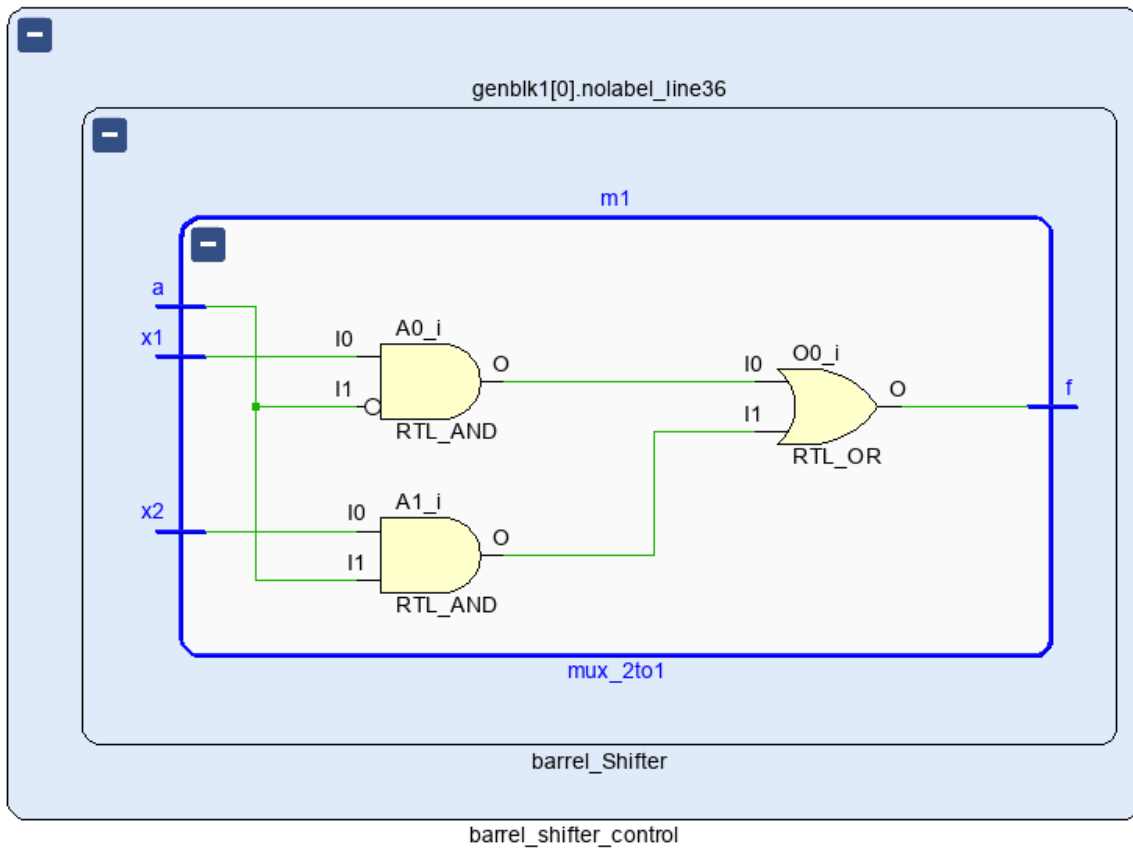

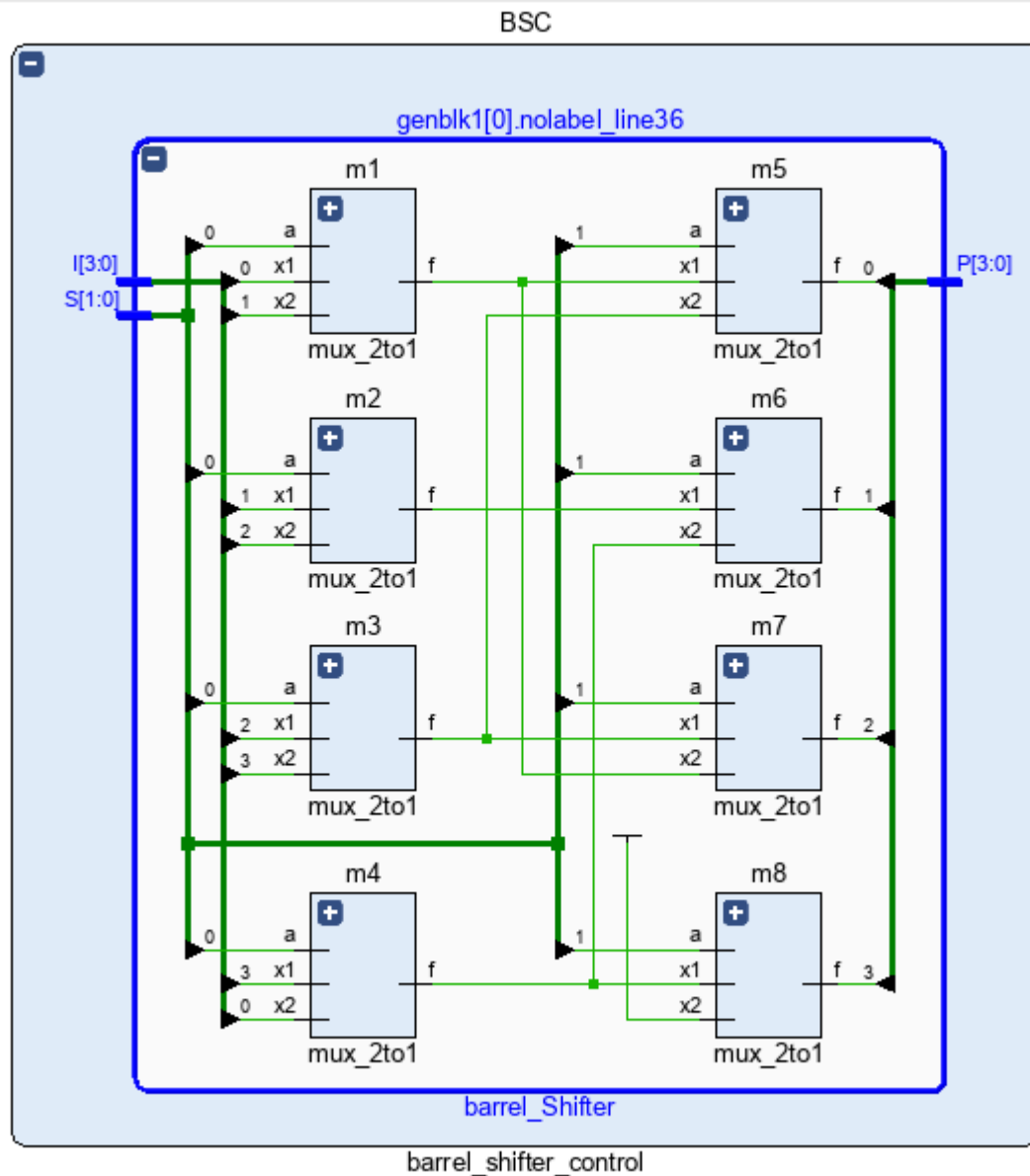


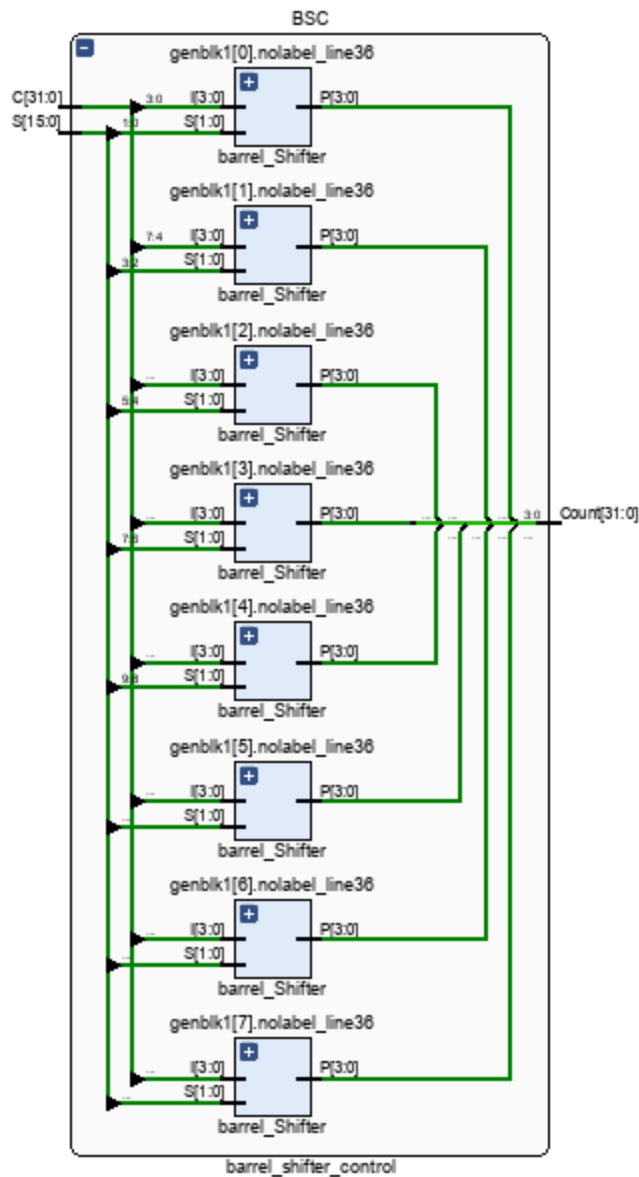4-bit barrel shifter uses 2 multiplexers however for our implementation, total muxes used was 8 multiplexers due to using the number of displays



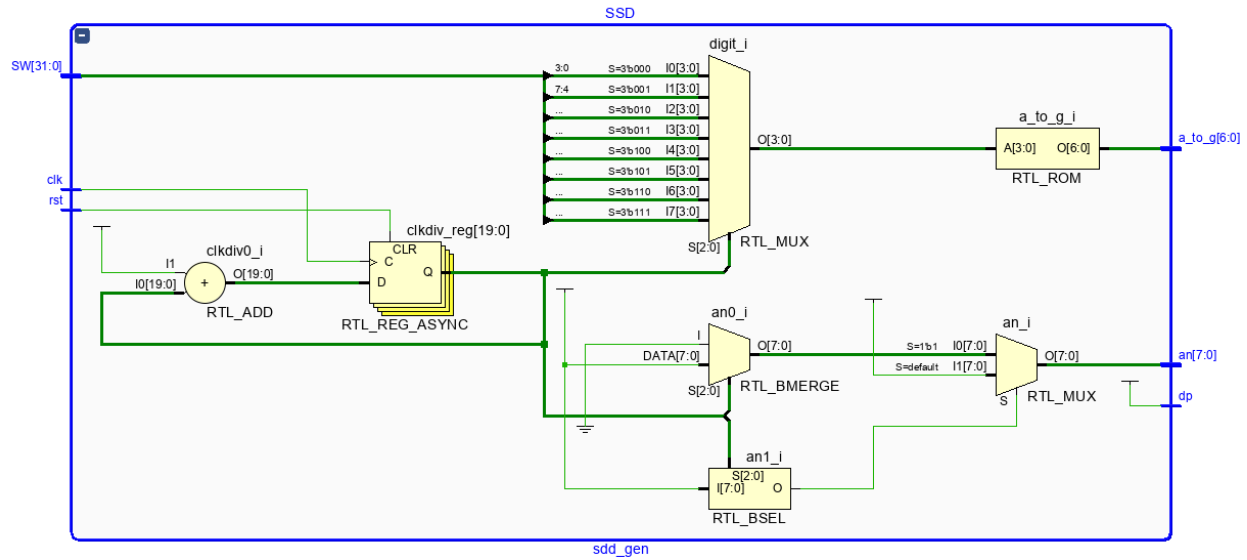

## Power Usage

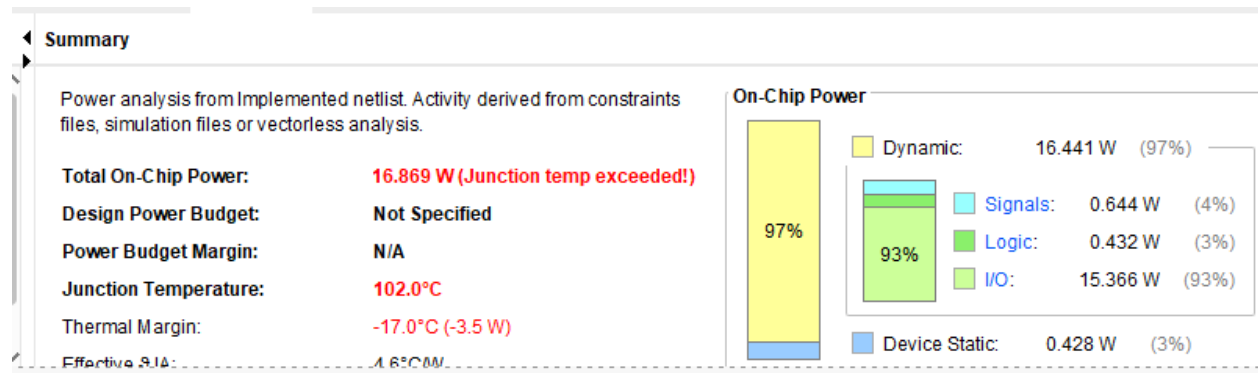

## Post-Implementation Resource Utilization

Name	Constraints	Status	WNS	TNS	WHS	THS	TPWS	Total Power	Failed Routes	LUT	FF	BRAM	URAM	DSP	Start	Elapsed	R
✓ synth_1	constrs_1	synth_design Complete!								126	95	0.0	0	0	11/22/21, 11:05 PM	00:00:28	V
✓ impl_1	constrs_1	write_bitstream Complete!	NA	NA	NA	NA	NA	16.869	0	126	95	0.0	0	0	11/22/21, 11:05 PM	00:01:02	V